



**Faculty of Engineering & Technology  
Electrical & Computer Engineering Department**

**CIRCUIT ANALYSIS ENEE2304**

**PSpice Project**

---

**Prepared by:**

Maha Maher Mali

1200746

**Instructor:** Dr. Hakam Shehadeh

**Section:** 1

**Date:** 14/6/2022

## Contents

Question 1 .....	4
Question 2 .....	5
Part A: .....	5
Part B.....	7
Part c:.....	8
Part D:.....	9

## Table of Figures

Figure 1: circuit for Question one .....	4
Figure 2: circuit for Q2 part A .....	5
Figure 3: The simulation Q2 part A.....	6
Figure 4: circuit for Q2 part B .....	7
Figure 5: The simulation Q2 part B.....	7
Figure 6 :circuit for Q2 part C .....	8
Figure 7: The simulation Q2 part C.....	8
Figure 8:Average power .....	9

## Question 1

Construct a PSPICE schematic for the circuit shown in the figure below. Simulate the schematic and show voltages at each node and current in each branch.

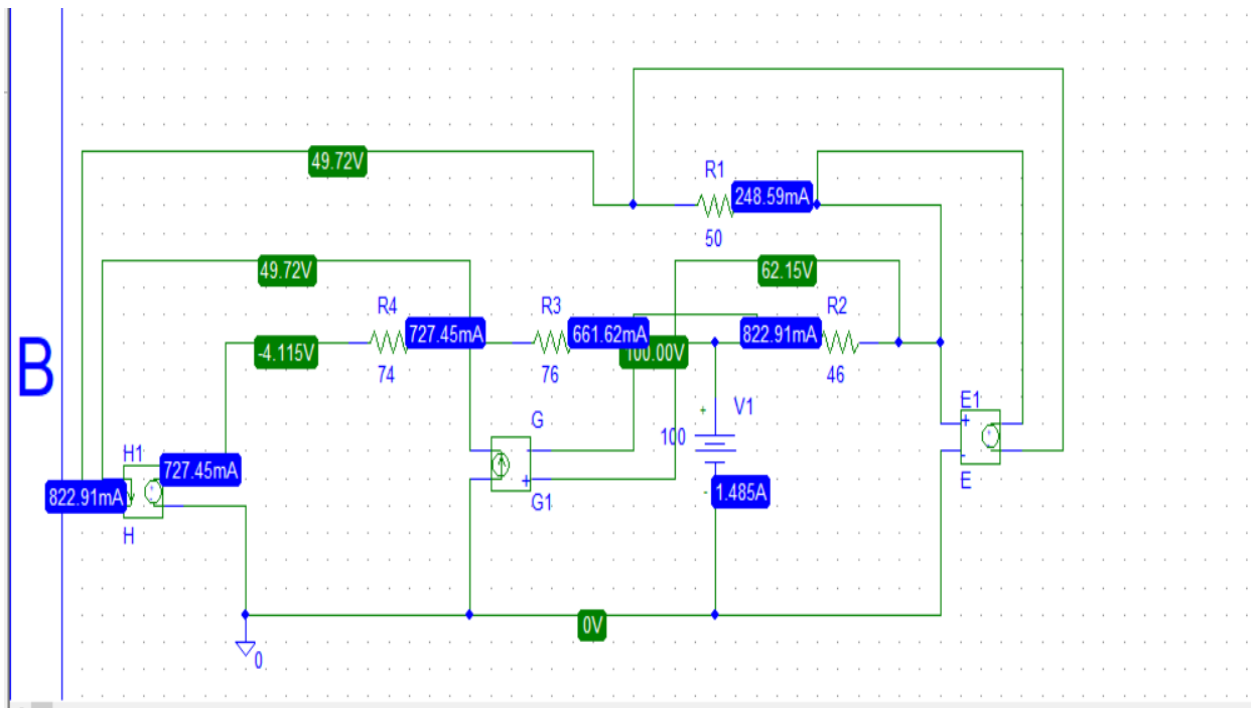
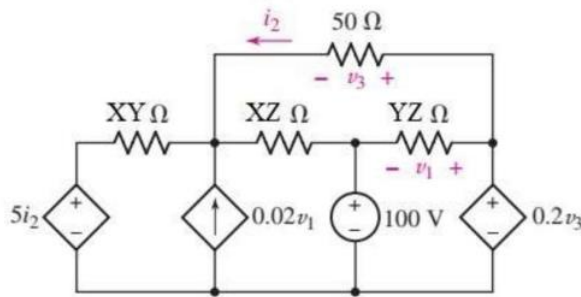


Figure 1: circuit for Question one

For  $5i_2$  I used the current controlled voltage source (H) in PSpice, and for  $0.2v_3$  I used voltage-controlled voltage source (E) in PSpice, and for  $0.02v_1$  I used voltage controlled current source.

## Question 2

The circuit shown in Figure below has two inputs,  $v_s(t)$  and  $i_s(t)$ , and one output,  $v(t)$ . When inputs are given by  $V_s(t) = V_m \sin 6t$  V and  $i_s(t) = I_m$  A the output will be  $v_o(t) = A \sin(6t + \theta) + B$  V

3Linearity requires that A be proportional to  $V_m$  and that B be proportional to  $I_m$ . Consequently, we can write  $A = k_1 V_m$  and  $B = k_2 I_m$ , where  $k_1$  and  $k_2$  are constants yet to be determined.


(a) Use PSpice to determine the value of  $k_1$  by simulating the circuit, using  $V_m = 1$  V and  $I_m = 0$ .

(b) Use PSpice to determine the value of  $k_2$  by simulating the circuit, using  $V_m = 0$  V and  $I_m = 1$ .

(c) Knowing  $k_1$  and  $k_2$ , specify the values of  $V_m$  and  $I_m$  that are required to cause  $v_o(t) = 5 \sin(6t + \theta) + 5$  V.

Simulate the circuit, using PSpice to verify the specified values of  $V_m$  and  $I_m$ .

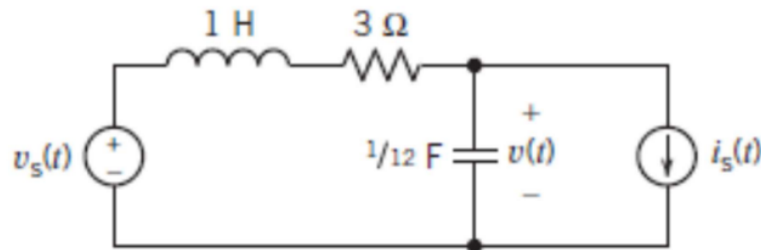(d) Determine the average power delivered by  $v_s(t)$  using Pspice.



Part A:

Circuit

$V_m = 1$  V,  $I_m = 0$  A


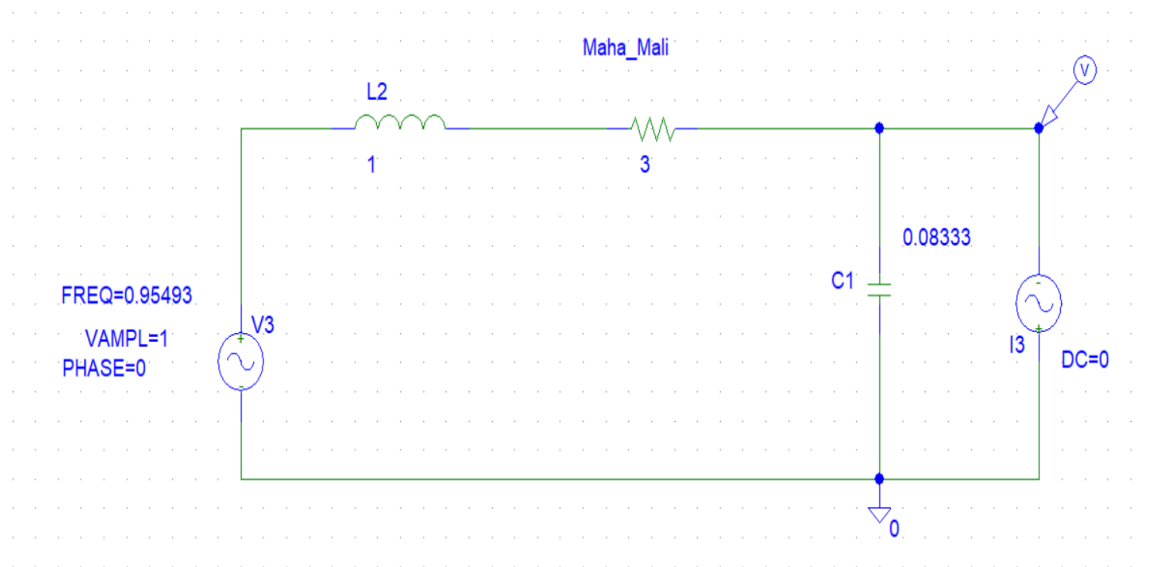


Figure 2: circuit for Q2 part A

The simulation:

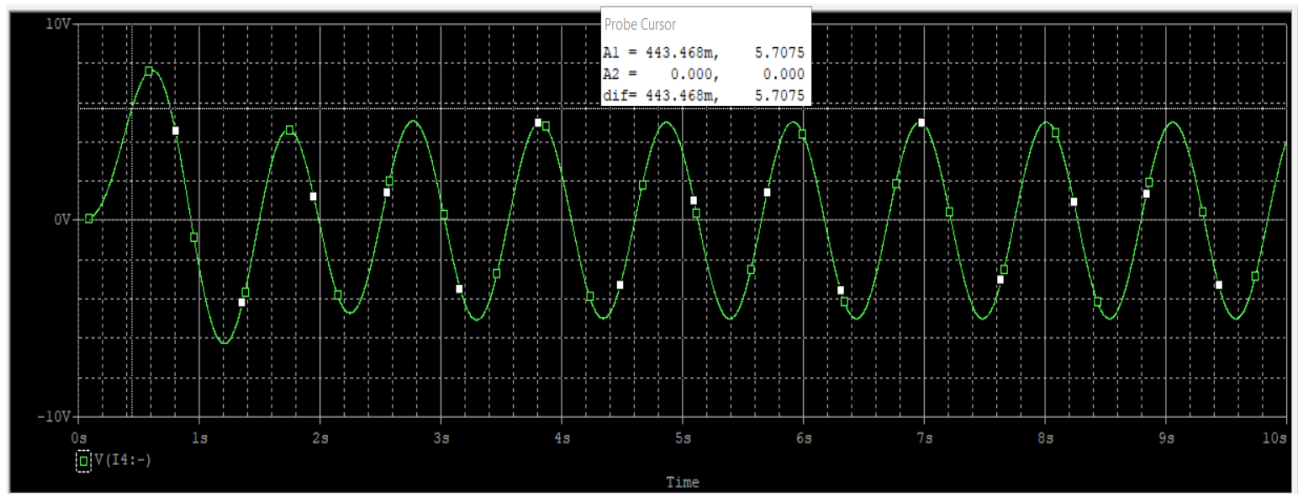

*Figure 3: The simulation Q2 part A*

**K1=0.4 V/A**

## Part B

### Circuit

$V_m=0\text{V}$ ,  $I_m=0\text{A}$

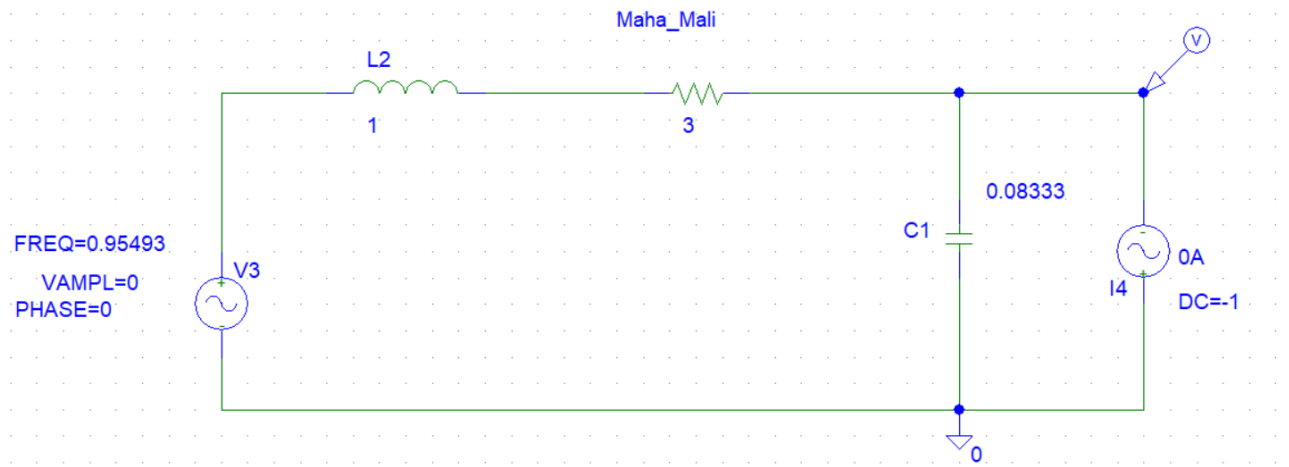


Figure 4: circuit for Q2 part B

The simulation:

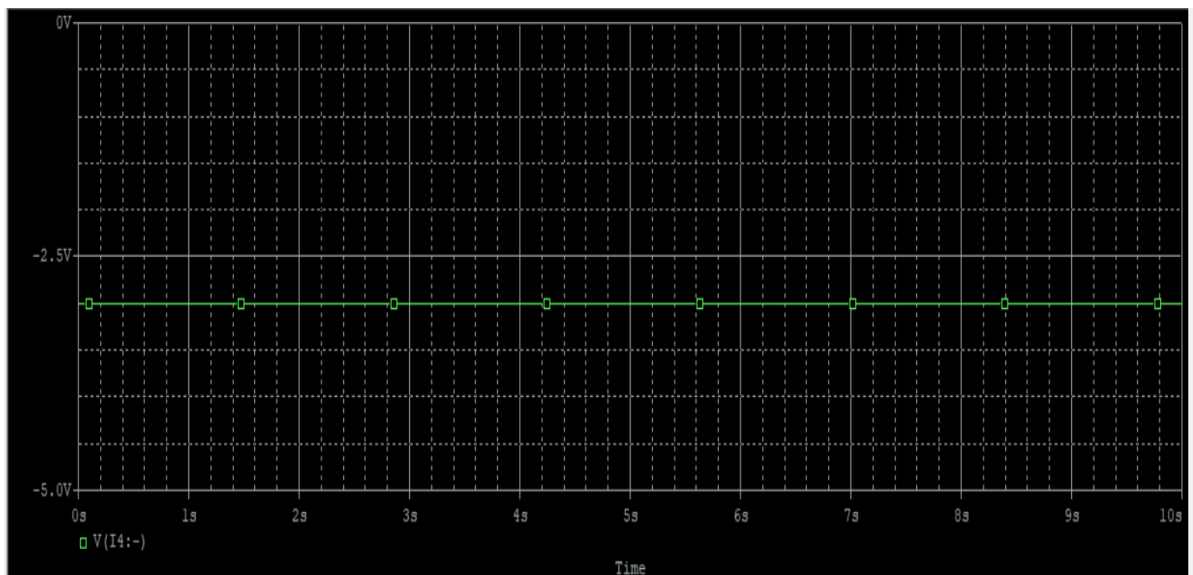


Figure 5: The simulation Q2 part B

$K_2=-3\text{ V/A}$

## Part c:

### Circuit

$$V_m = 5/k_1 = 5/0.405 = 12.35 \text{ V}, \quad I_m = 5/k_2 = 5/-3 = -1.67 \text{ A}$$

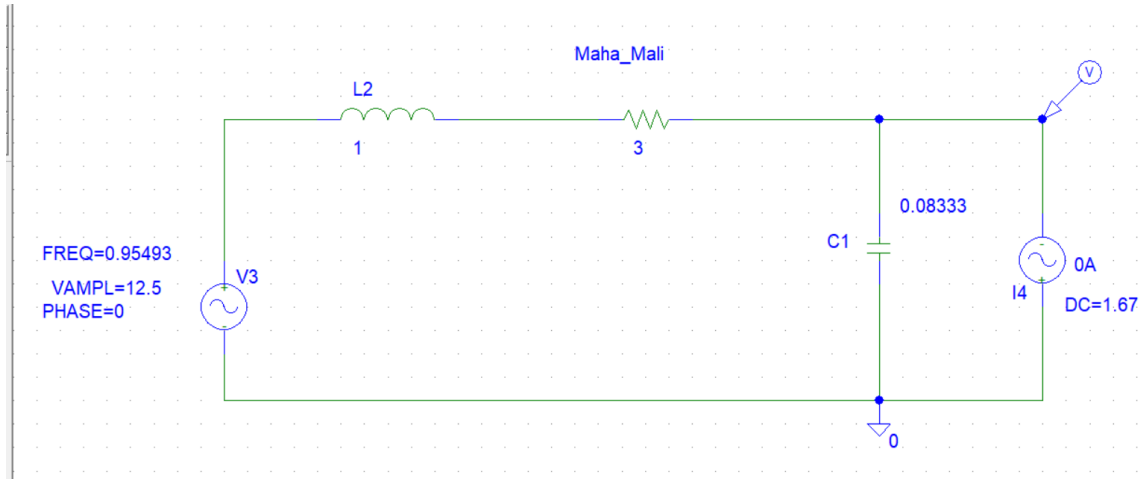


Figure 6 :circuit for Q2 part C

### The simulation:


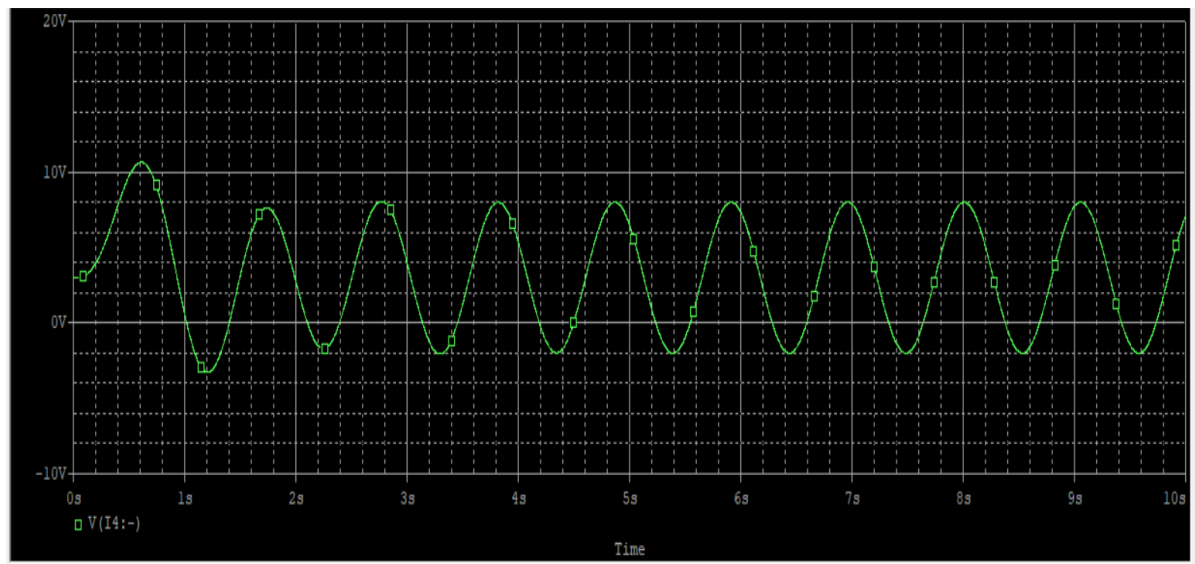


Figure 7: The simulation Q2 part C

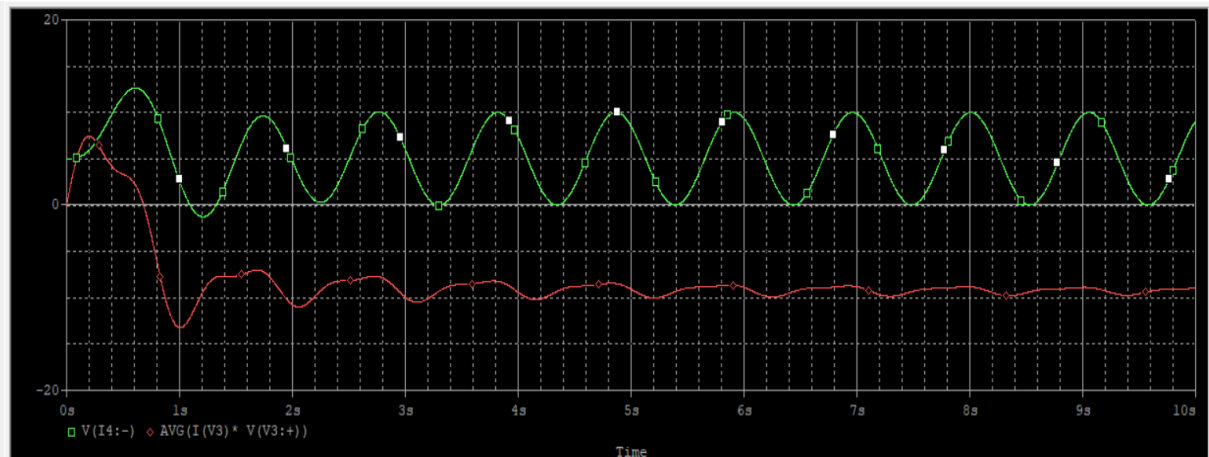

Part D:



*Figure 8: Average power*

$$P = 0.5 V_m I_m = 0.5 (12.5) (-1.67) = -10.418 \text{ watt (deliver power)}$$